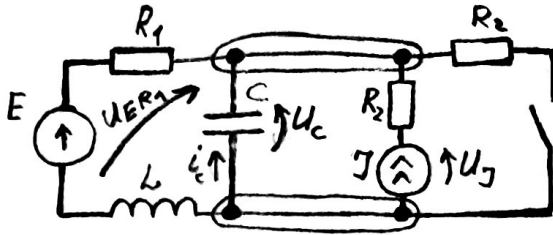


Вариант 14




Исходные данные:

$$E = 104 \text{ В}; J = 1,04 \text{ В}; L = 4 \cdot 10^{-3} \text{ Гн}; \\ R_1 = 2 \text{ Ом}; R_2 = 50 \text{ Ом}; C = 40 \cdot 10^{-6} \text{ Ф}.$$

ТЗ: $U_C(t), i_C(t), U_J(t), U_{R_1}(t), \tau$?

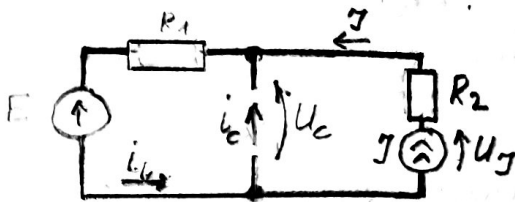1. Определение начальных условий ($t=0$):

Т.к. вх. воздействие постоянное, конденсатор \rightarrow разрыв;
катушка \rightarrow заморозка.



$$i_C(0_-) = 0,$$


$$U_C(0_-) = U_{R_2 J}(0_-)$$

$$J(R_1 + R_2) = U_J - E \Rightarrow U_J(0_-) = J(R_1 + R_2) + E = 1,04 \cdot 52 + 104 = 158,08 \text{ В}$$

$$U_C(0_-) = U_{R_2 J}(0_-) = J R_2 + U_J(0_-) = 1,04 \cdot 50 + 158,08 = 210,08 \text{ В}$$

$$i_L(0_-) = J = 1,04 \text{ А}.$$

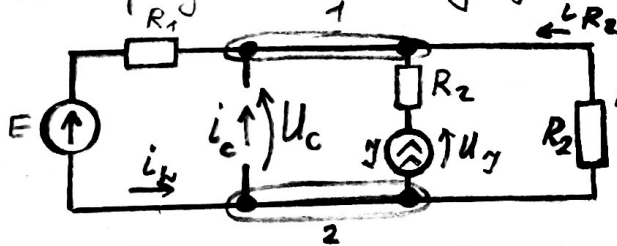2. Определение вынужденной составляющей ($t=\infty$):



$$i_C(\infty) = 0,$$

$$U_C(\infty) = \frac{\sum \frac{E_i}{R_i} + \sum J_i}{\sum \frac{1}{R_i}} =$$


$$= \frac{\frac{E}{R_1} + J}{\frac{1}{R_1} + \frac{2}{R_2}} = \frac{\frac{104}{2} + 1,04}{\frac{1}{2} + \frac{2}{50}} = 98,2 \text{ В}$$

$$i_L = J + i_{R_2} ; i_{R_2}(\infty) = \frac{U_{R_2}(\infty)}{R_2} = \frac{U_C(\infty)}{R_2} = \frac{98,2}{50} = 1,964 \text{ А}$$

$$i_L(\infty) = 1,04 + 1,964 = 3,004 \text{ А}$$

$$U_{R_2}(\infty) = J R_2 + U_J(\infty) \Rightarrow U_J(\infty) = U_{R_2}(\infty) - J R_2 = 98,2 - 1,04 \cdot 50 = 46,2 \text{ В}.$$

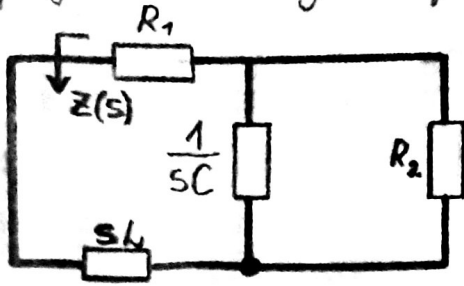3. Определение вида переходного процесса:



$$Z(s) = R_1 + \frac{\frac{1}{sC} \cdot R_2}{\frac{1}{sC} + R_2} + sL = 0$$

$$s^2 + s \cdot \left(\frac{R_1}{L} + \frac{1}{R_2 C} \right) + \frac{R_1 + R_2}{L R_2 C} = 0$$

$$s^2 + 1000s + 6500000 = 0$$

$$D = -25000000 < 0$$

$$s_{1,2} = \delta \pm j\omega = -500 \pm 2500j$$

$$s(t) = s(\infty) + e^{\delta t} (A_1 \cos \omega t + A_2 \sin \omega t)$$

$$u_c(t) = 98,2 + e^{-500t} (A_1 \cos 2500t + A_2 \sin 2500t)$$

4. Нахождение коэффициентов A_1 и A_2 :

Законы коммутации:


$$u_c(0_-) = u_c(0_+); \quad i_L(0_-) = i_L(0_+).$$

$$u_c(0_+) = 98,2 + e^{-500 \cdot 0} (A_1 \cos 2500 \cdot 0 + A_2 \sin 2500 \cdot 0) = u_c(0_-) = 210,08 \text{ В}$$

$$98,2 + A_1 = 210,08$$

$$A_1 = 111,88$$

Чтобы найти A_2 , надо найти $i_c(0_+)$:

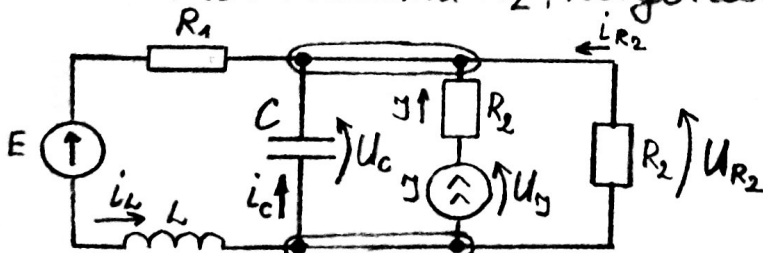

$$i_c(0_+) + J + i_{R_2}(0_+) = i_L(0_+)$$

$$i_c(0_+) = i_L(0_-) - J - \frac{u_c(0_-)}{R_2} =$$

$$= 1,04 - 1,04 - \frac{210,08}{50} = -4,202 \text{ А}$$

$$\begin{aligned} i_{R_2}(0_+) &= \frac{u_{R_2}(0_+)}{R_2} = \frac{u_c(0_+)}{R_2} \\ &= \frac{u_c(0_-)}{R_2} \\ i_L(0_+) &= i_L(0_-) \end{aligned}$$

$$\frac{dU_c(t)}{dt} = -500 e^{-500t} (A_1 \cos 2500t + A_2 \sin 2500t) + e^{-500t} \cdot [A_1 \cdot 2500 \cdot (-\sin 2500t) + A_2 \cdot 2500 \cdot \cos 2500t] = \frac{i_c(t)}{C}$$

$$\frac{i_c(0_+)}{C} = -500 \cdot 1 (111,88 \cdot 1 + A_2 \cdot 0) + 1 \cdot (A_1 \cdot 0 + A_2 \cdot 2500 \cdot 1) = \frac{-4,202}{40 \cdot 10^{-6}}$$

$$A_2 = -19,644$$

$$U_c(t) = U_c(\infty) + e^{\delta t} \sqrt{A_1^2 + A_2^2} \sin(\omega t + \arctg \frac{A_2}{A_1})$$

$$\underline{U_c(t)} = 98,2 + e^{-500t} \cdot 113,591 \sin(2500t - 80,041)$$

$$i_c(t) = \frac{dU_c(t)}{dt} \cdot C$$

$$\underline{i_c(t)} = e^{-500t} (-105050 \cos 2500t - 269878 \sin 2500t)$$

$$\mathcal{U}R_2 + U_g = U_c$$

$$U_g(t) = U_c(t) - \mathcal{U}R_2$$

$$\underline{U_g(t)} = 46,2 + e^{-500t} \cdot 113,591 \sin(2500t - 80,041)$$

$$U_{ER_1}(\infty) = E - i_c(\infty)R_1 = 104 - 3,004 \cdot 2 = 97,992.$$

$$\underline{U_{ER_1}(t)} = 97,992 + e^{-500t} \cdot 113,591 \sin(2500t - 80,041)$$

$$\tau = \frac{1}{181} = \frac{1}{500}$$